



COMSATS University Islamabad, Lahore Campus
Department of Electrical and Computer Engineering

☐ Sessional-1 ☐ Sessional-II ☒ **Terminal Examination – SPRING 2021**

Course Title:	Microprocessor System and Interfacing			Course Code:	CPE/EEE 342	Credit Hours:	4(3,1)
Course Instructor:	Dr. Abbas Javed/Dr. Naeem Shehzad			Program Name:	BCE, BEE		
Semester:	6 th	Batch:	FA18	Section:	A & B	Date:	July 13, 2021
Time Allowed:	180 Minutes			Maximum Marks:	50		
Student's Name:				Reg. No.	CIIT/	/LHR	

Important Instructions / Guidelines:

- This is an open book examination.
- The exam is online. The time limit to solve this exam is 3-hour and extra 15 mins are given to upload your exam.
- Write your name and registration number in the above-mentioned space using Microsoft Word.
- Solve the questions on your notebook and insert the images of your solution at the end of the question paper.
- Save your exam file in the following format and submit your exam file on CUonline:
- XXE342-S-I-FA1X-00X.PDF

Question 1:

[CLO1-C4-PO3] [5]

Analyze the following assembly language code using the knowledge of 8086 programming model, addressing mode and assembly language programming concepts. You are required to show the value of updated registers after execution of each instruction:

```
MOV DX, 02000H
MOV SP, DX
MOV DX, 0A000H
MOV SS, DX
MOV AX, 01D00H
MOV BX, 2000H
PUSH AX
PUSH BX
ADD AX, BX
PUSH AX
POP CX
POP DX
```

MST Terminal Exam Solution

Q.1) 1) DX 20 00

2) SP 20 00

3) DX 0A0 00

4) SS 40 00

5) AX 1D 00

6) BX 20 00

7) A000: 1FFE 1D 00 SP 1FFE

A000: 1FFC 2000 SP 1FFC

AX → 3D 00

A000: 1FFA 3D 00 SP 1FFA

CX · 3D 00 SP 1FFC

DX 20 00 SP 1FFE

Integrate total of 32KB SRAM and total of 16 KB EPROM with 8086 CPU. Available SRAM memory circuits are 4KB chips only and EPROM memory circuits are 2 KB only. Starting address for EPROM is X0000 H and choose suitable starting address for SRAM. Where X is the non-zero least significant digit of your registration number. Draw completely labelled schematic diagram of memory integration with CPU and mention starting and ending address of each chip.

2) Integrate 32 KB SRAM \rightarrow available chip 4 KB
 16 KB EPROM \rightarrow available 2 KB
 2 KB \rightarrow A1 - A11

	A ₁₉	A ₁₈	A ₁₇	A ₁₆	A ₁₅	A ₁₄	A ₁₃	A ₁₂	A ₁₁	A ₁₀	A ₉	A ₈	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
9000	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
90FF	1	0	0	1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	0
90FF	1	0	0	1	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1
1000	1	0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
11FF	1	0	0	1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	0
11FF	1	0	0	1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1
1FF	1	0	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1FF	1	0	0	1	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	0
2FF	1	0	0	1	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1
2FF	1	0	0	1	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1
3FF	1	0	0	1	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0
3FF	1	0	0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	0
3FF	1	0	0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1

A₁₄ - A₁₉ \rightarrow CS.

A₁₂ - A₁₃ \rightarrow select line of 2-4 decoder

A₁ - A₁₁ \rightarrow 2 KB EPROM.

32KB SRAM.

A19 A18 A17 A16 A15 A14 A13 A12 A11 A10 A9 A8 A7 A6 A5 A4 A3 A2 A1 A0														A0														

Integrate 8254 timer with 8086 microprocessor and program counter 1 so that it generates a continuous wave of X00 KHz at OUT1. Program counter 2 so that it generates an interrupt after every X00 micro-seconds where X is non zero least significant digit of your registration number. (For a student with registration number Fa18-BCE-107, X is 7). You are free to choose any suitable address for 8254 timer and suitable input clock frequency.

Q.3

for Roll number with last digit 9.

```
MOV DX, 706H
MOV AL, 0110101
OUT DX, AL
```

```
MOV DX, 706H
MOV AL, 00110001
OUT DX, AL
```

```
MOV DX, 702H
MOV AL, 00
OUT DX, AL
```

```
MOV AL, 00
OUT DX, AL
```

$$\text{clock} = \frac{\text{input frequency}}{\text{divide factor}}$$

$$\text{count} = \frac{9 \text{ MHz}}{900 \text{ kHz}}$$

$$\text{count} = 90.$$

$$\text{Count} = 900$$

$$\text{clock} =$$

```
MOV DX, 704H
```

```
MOV AL, 00
```


```
OUT DX, AL
```

```
MOV AL, 09
```

```
OUT DX, AL
```


Integrate 4 coil stepper motor in wave drive mode with 8086 microprocessor using programmable peripheral interface (PPI). Stepper motor should rotate 'n' steps in clockwise direction, where n will be entered by the user through 4 slide switches. Integrate 4 slide switches with PPI to input 4-bit data. Write an assembly program to stepper motor and slide switches and draw a schematic diagram. Choose suitable addresses for peripheral interfacing.

Q.4.

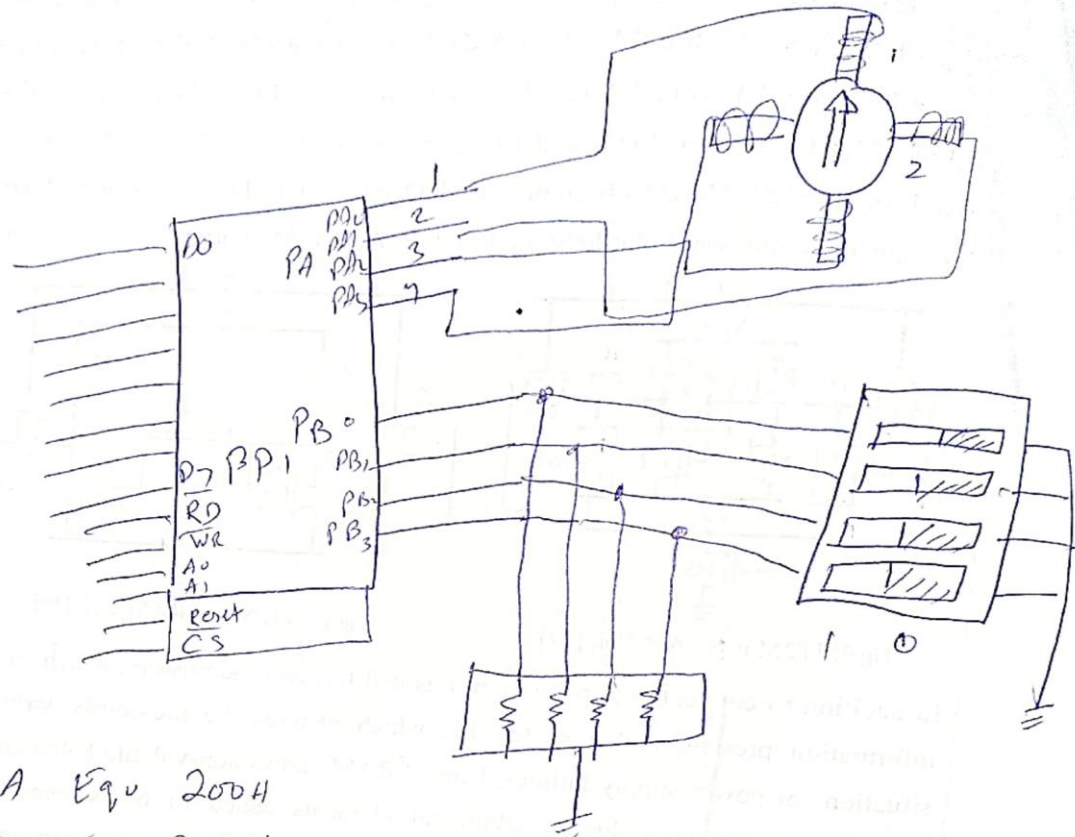

Port A Equ 200H
Port B Equ 202H
Port C Equ 204H
PPI

1 0 0 0 0 0 1 0 → 82H

MOV AL, 82H
MOV DX, 206H
OUT DX, AL


1 C₇ C₃ C₂ C₁ C₄ C₂ C₂ C₁
2 0 0 0 1 0 0 0 1

IN AL, PortB → MOV Slide Switch input to AL

MOV CX, AX

MOV AL, POS

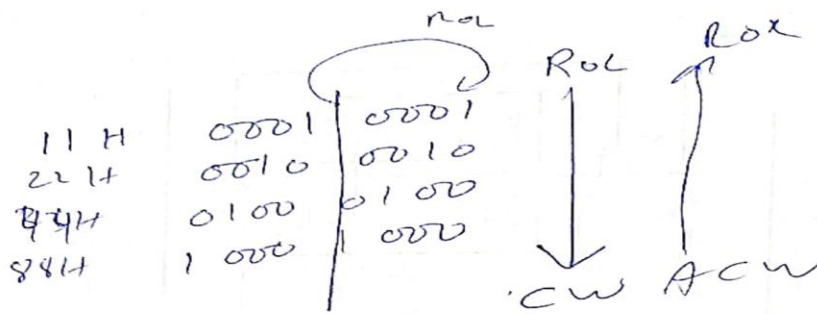Current angular location
Stored at location POS (is many)
Pos 11H, 22H, 44H 88H



Repat

ROR AL, 1

Out Port A, AL
Call Delay.

Until CXZ

MOV POS, AL

RET

Question 5:

[CLO3-C5-PLO3][5+10]

Design a 8088 microprocessor based temperature controller for maintaining indoor thermal comfort. Temperature controller should control the HVAC to maintain the cooling setpoint entered by the occupant. Temperature controller should turn OFF the HVAC when indoor room temperature is equal to or less than cooling setpoint and turn ON the HVAC when the room temperature is greater than cooling setpoint. As a design engineer, you are required to implement the following tasks:

1. Interface a LM 35 temperature sensor using Analog to Digital Converter (ADC) with 8088 microprocessor. LM35 is a temperature sensor which can measure temperature in the range of -55°C to 150°C. The output voltage of this 3 pin temperature sensor is directly proportional to the ambient temperature and is given by the formula:

$$V_{out} = K * T$$

Where

K = 10 mv/°C

T = ambient temperature


For a temperature range of 0-100 °C, the output varies from 0-1 V with step of 10 mv. Starting address of the ADC is your registration number. (For a student with registration number Fa18-BCE-107, the starting address will be 107H)

2. Integrate a suitable peripheral for allowing the occupant to enter the required cooling setpoint. Starting address of PPI is 0X000 H where X is least significant digit of your registration number. (For a student with registration number Fa18-BCE-107, the starting address will be 07000H)
3. Integrate a suitable peripheral for displaying the current room temperature.
4. Control the HVAC using digital switch connected to the digital output of the microprocessor.

a) Draw a completely labelled circuit diagram of temperature controller

b) Write an Assembly code for implementing the temperature controller.

Q.5

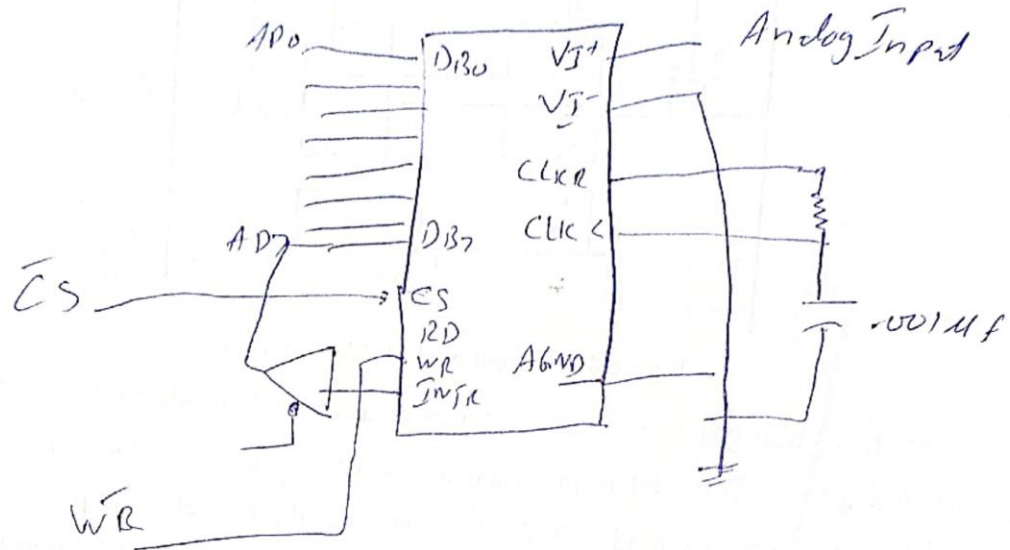

For Register ID F00BCE-0
ADCX Proc New.

Out 90H, AL

ADCX1:

IN AL, 92H

Test AL, 80H

JNZ ADCX,

IN AL, 90H

RET

ADCX ENDP

Resolution $\frac{5.1}{255} = 0.02V = 20mV$

For $0-100^{\circ}C$

ADC Value changes from 0-50

Multiply by 2 to get actual temp

Let's suppose $26^{\circ}C$ is cooling setpoint

ADC value is 13 for $26^{\circ}C$ temp

TempSet EQU 13

CALL ADCX
CALL KEY

CMP AL, TempSet

~~JGE~~ HVAC ON

~~JGE~~ JGE HVAC ON

JLE HVAC OFF

HVAC ON:

OUT 100H, 01H.

CALL Write

HVAC OFF

OUT 100H, 00H.

CALL Write

Assume HVAC control
switch interfaced at
100H.

2) Open Ended- Student may use keypad or slide switches/buttons

Buttons

IN AL, DX

Keypads

assembly language version;

;KEY scans the keyboard and returns the key code in AL.

COLS EQU 4

ROWS EQU 4

PORTA EQU 50H

PORTB EQU 51H

KEY PROC NEAR USES CX BX

MOV BL,FFH ;compute row mask

SHL BL,ROWS

MOV AL,0

OUT PORTB,AL ;place zeros on Port B

.REPEAT ;wait for release

.REPEAT

CALL SCAN

.UNTIL ZERO?

CALL DELAY10

CALL SCAN

.UNTIL ZERO?

.REPEAT ;wait for key

.REPEAT

CALL SCAN

.UNTIL !ZERO?

CALL DELAY10

CALL SCAN

.UNTIL !ZERO?

MOV CX,00FEH

.WHILE 1 ;find column

MOV AL,CL

OUT PORTB,AL

CALL SHORTDELAY ;see text

CALL SCAN

.BREAK !ZERO?

ADD CH,COLS

ROL CL,1

.ENDW

.WHILE 1 ;find row

SHR AL,1

.BREAK .IF !CARRY?

INC CH

.ENDW

MOV AL,CH ;get key code

RET

```

KEY ENDP
SCAN PROC NEAR
    IN AL,PORTA ;read rows
    OR AL,BL
    CMP AL,0FFH ;test for no keys
    RET
SCAN ENDP

```

```

3) USE LCD to Display
WRITE PROC NEAR
MOV AL,BL ;BL to Port A
MOV DX,PORTA_ADDRESS
OUT DX,AL
MOV AL,0 ;write ASCII
MOV DX,PORTB_ADDRESS
OUT DX,AL
OR AL,00000100B ;Set E bit
OUT DX,AL ;send to Port B
AND AL,11111011B ;Clear E bit
NOP ;a small delay
NOP
OUT DX,AL ;send to Port B
CALL BUSY ;wait for completion
RET
WRITE ENDP

```